
Lime Microsystems Limited

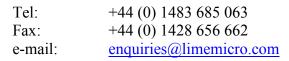Surrey Tech Centre Occam Road The Surrey Research Park Guildford, Surrey GU2 7YG United Kingdom





LMS7002M power supply connection

- Application note - (Version 01, Revision 01)

Document version: 01
Document revision: 01

Last modified: 24/12/2015 13:55:00

Contents

1. Po	ower pins and supply mode description	3
1.1		3
1.2	Power pin description	5
1.3	Supply option description	
2. Sı	upply pin connection	7
	Connection to multiple external supply sources	
	Connection to single external supply	
3. R	ecommendations for board design	11
3.1	Power supply pin connection	11
	TX power amplifier supply connection	

Revision History

Version 1r00 Released: 30 Nov, 2015

Initial version.

1

Power pins and supply mode description

1.1 Overview

LMS7002M chip power supply pins can be separated into two groups:

- 1. Low voltage power supply pins. Supply line voltage 1.25V and 1.4V;
- 2. High voltage power supply pins. Supply line voltage 1.8V (optional additional 3.3V for digital input/output drivers).

LMS7002M power supply groups are shown in Figure 1. There are three groups (J5-K6; L5-K2; F8-D6) of pins that need external connections for the LMS7002M to work properly if internal low-dropout regulators (LDOs) are used. These pins are highlighted red in Figure 1. It should be noted, that four additional pin groups, in high (AH30-W33-W31; H32-T32) and low (AE29-AA29; R31-L33) voltage supply chains are connected internally. These pins are highlighted green in Figure 1.

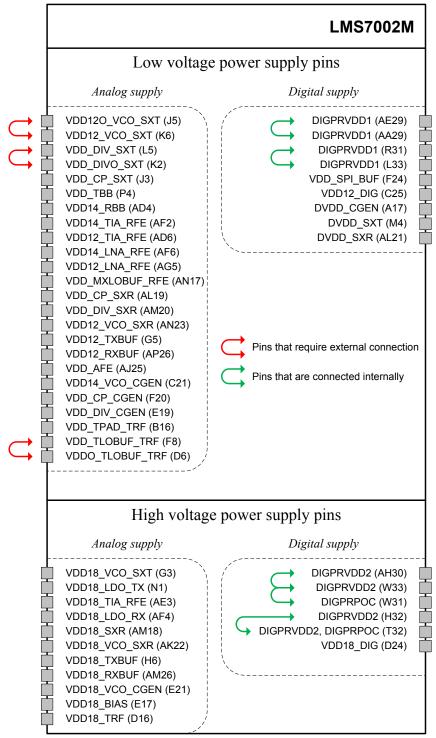


Figure 1. LMS7002M power supply pin diagram

1.2 Power pin description

A list of power supply pins and their description is given in Table 1.The pins are sorted by their appropriate connections to various analog and digital blocks.

Table 1: LMS7002M power pin description

Block D		Table 1: LMS/002M power pin description Pin Pin Supply Supply Internal Pin Discharge Control Pin description							
Ke	Block		Pin Name				Pin description		
Transmitter (TX Synthesizer (SXR)		J5	VDD12O_VCO_SXT	A		Vos	SXT VCO LDO output		
Symbolizer Sym		K6	VDD12_VCO_SXT	A	1.25	1 68	Power supply for SXT VCO		
Synthesizer Color	Transmitter (TX)	L5	VDD_DIV_SXT	A	1.25-1.4 ^B	V	Power supply for SXT divider circuits		
SXR 3	synthesizer	K2	VDDO DIV SXT	A	1.25-1.4 ^B	y es			
M4	(SXR)			A		Yes			
G3	, ,	M4		D	1.25	Yes			
TX radio frequency (RF) F8 VDD TLOBUE TRF A 1.25 Yes Power supply for TRF power amplifier circuits F8 VDD TLOBUE TRF A 1.25 Yes Power supply for TRF power amplifier circuits TRF RF path circuit LDO output TRF RF path circuit TRF RF path circuit LDO output TRF RF path circuit TRF RF path circ				A					
Tx radio FR									
Incquency (RF) D6		F8		A	1.25				
Translog base band (TBB) Tx Color bullet Tx Tx Tx Tx Tx Tx Tx T		D6	VDDO TLOBUF TRF	A	1.25	Yes			
TX analog base band (TBB)	front-end (TRF)	D16				No			
TX clock buffer (TXBUF)				A	1.25				
Receiver (RX)		G5	VDD12 TXBUF	A	1.25	Yes	Power supply for TXBUF		
Receiver (RX) AND 21 VCO SXR				A	1.8-3.3 ^C	No	11 7		
Receiver (RX) synthesizer RX Synthesizer RX Synthesizer RX Synthesizer RX RX RX RX RX RX RX R	/	AN23		A		Yes			
Synthesizer	Receiver (RX)								
(SXR)			VDD CP SXR						
RX RF front-end (RFE)	-								
AF6 VDD12 LNA RFE A 1.4 Yes Power supply for RX LNA	(2222)						Power supply for SXR VCO		
RX RF front-end (RFE)									
AFE AD6 VDD12 TIA RFE A 1.4 Yes Power supply for RX TIA									
AD6	RX RF front-end								
AN17 VDD_MXLOBUF_RFE A 1.25-1.4 Yes Power supply for RX RF path circuits	(RFE)						Power supply for RX TIA and some RRR control blocks		
RX analog base band (RBB)									
RX clock buffer (RXBUF)							***		
RXBUF AM26 VDD18 RXBUF A 1.8-3.3° No Power supply for RXBUF		AP26	VDD12 RXBUF	A	1.25	Yes	Power supply for RXBUF		
C21					1.8-3.3 ^C				
Clock generator (CGEN)	/			A	1.4				
CIGEN) (CGEN)									
Ali	_								
RX TSP	(CGEN)								
Analog front-end (AFE)									
Serial port interface (SPI) F24 VDD_SPI_BUF D 1.25 Yes Power supply for SPI core buffers					1.25		***		
interface (SPI) TX Transceiver Signal Processor (TSP) RX TSP R31 DIGPRVDD1 D 1.25 Bigital pad I/O drivers and power-on (POC) circuits T32 DIGPRVDD2 D 1.8-3.3D DIGPRVDD2 T32 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T34 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T35 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T36 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T37 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T38 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T39 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T30 DIGPRVDD2 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 T32 DIGPRVDD2 DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 D 1.8-3.3D No DIGPRVDD2 DIGPRVD2 D 1.8-3.3D No DIGPRVDD2 DIGPRVD2 D 1.8-3.3D No DIGPRVDD2 DIGPRVD2 D 1.8-3.3D No DIGPRVD2 DIG		E17	VDD18 BIAS	A	1.8	No	Power supply for BIAS block		
TX Transceiver Signal Processor (TSP) RX TSP R31 DIGPRVDD1 D 1.25 L33 DIGPRVDD1 D 1.25 Digital pad I/O drivers and power-on (POC) circuits N1 VDD18_LDO_TX N1 VDD18_LDO_TX AE29 DIGPRVDD1 D 1.25 Yes Power supply for I/O pre-drivers, TX TSP, digital data and clock buffers Power supply for I/O pre-drivers, RX TSP, microcontroller (MCU), LimeLight M, SPI core Power supply for I/O pre-drivers, RX TSP, microcontroller (MCU), LimeLight M, SPI core Power supply for I/O pre-drivers, RX TSP, microcontroller (MCU), LimeLight M, SPI core Power supply for I/O post-drivers, POC circuits Power supply for I/O post-drivers, POC circuits Power supply for TBB, SXT, TRF LDO's, TBB external input switch control AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for Various digital circuits	Serial port	E24	VDD CDI DIJE	D	1.25	Vac	Davier supply for CDI care buffers		
Signal Processor (TSP) RX TSP R31 DIGPRVDD1 D 1.25 B31 DIGPRVDD1 D 1.25 RX TSP AH30 DIGPRVDD1 D 1.25 B133 DIGPRVDD2 D 1.8-3.3 ^D Circuits B142 DIGPRVDD2 D 1.8-3.3 ^D B152 DIGPRVDD2 D 1.8-3.3 ^D B152 DIGPRVDD2 D 1.8-3.3 ^D B152 DIGPRVDD2 D 1.8-3.3 ^D B153 DIGPRVDD2 D 1.8-3.3 ^D B152 DIGPRVDD2 D 1.8-3.3 ^D B153 DIGPRVDD2 D 1.8-3.3 ^D B154 DIGPRVDD2 D 1.8-3.3 ^D B152 DIGPRVDD2 D 1.8-3.3 ^D B153 DIGPRVDD2 D 1.8-3.3 ^D B154 DIGPRVDD2 D 1.8-3.3 ^D B155 DIGPRVDD2 D 1.8-3.3 ^D B156 DIGPRVDD2 D 1.8-3.3 ^D B156 DIGPRVDD2 D 1.8-3.3 ^D B157 DIGPRVDD2 D 1.8-3.3 ^D B158 DIGPRVD2 D 1.8-3.3 ^D B158 D						res			
RX TSP R31 DIGPRVDD1 D 1.25 L33 DIGPRVDD1 D 1.25 Digital pad I/O drivers and power-on (POC) circuits N1 VDD18_LDO_TX Various R31 DIGPRVDD1 D 1.25 Power supply for I/O pre-drivers, RX TSP, microcontroller (MCU), LimeLight TM , SPI core Power supply for I/O pre-drivers, RX TSP, microcontroller (MCU), LimeLight TM , SPI core Power supply for I/O post-drivers, POC circuits No Power supply for I/O post-drivers, POC circuits Power supply for I/O post-drivers, POC circuits Power supply for I/O post-drivers, POC circuits Power supply for TBB, SXT, TRF LDO's, TBB external input switch control AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits	Signal Processor					Yes			
L33 DIGPRVDD1 D 1.25 microcontroller (MCU), LimeLight MCU, Lim	` '	R31	DIGPRVDD1	D	1 25		Power supply for I/O pre-drivers RX TSP		
Digital pad I/O drivers and power-on (POC) circuits No	RX TSP					Yes	microcontroller (MCI) LimeLight TM SPI core		
Digital pad I/O drivers and power-on (POC) circuits W33 DIGPRVDD2 D 1.8-3.3 ^D No H32 DIGPRVDD2 D 1.8-3.3 ^D No T32 DIGPRVDD2, DIGPRPOC D 1.8-3.3 ^D No Power supply for I/O post-drivers, POC circuits No Power supply for TBB, SXT, TRF LDO's, TBB external input switch control AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits							intercontroller (NICO), ElineElight , 51 Feore		
drivers and power-on (POC) circuits W31	Digital pad I/O					No			
power-on (POC) circuits H32	0 1					140			
circuits T32 DIGPRVDD2, DIGPRPOC D 1.8-3.3 ^D No Power supply for TBB, SXT, TRF LDO's, TBB external input switch control AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers Various AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits					1.0 3.3 1 8-3 3 ^D		Power supply for I/O post-drivers, POC circuits		
Various N1		1132		Ъ		No			
Various No Power supply for TBB, SXT, TRF LDO's, TBB external input switch control AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers Various AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits	Circuits	T32		D	1.0-3.3	110			
Various AE3 VDD18_TIA_RFE A 1.8 No Power supply for RFE, RBB, ADC external input buffers AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits		N1		A	1.8	No			
Various AF4 VDD18_LDO_RX A 1.8 No Power supply for RFE and RBB LDO's AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits	Various	AE3	VDD18 TIA RFE	A	1.8	No			
AM18 VDD18_SXR A 1.8 No Power supply for SXR and AFE LDOS's. C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits									
C25 VDD12_DIG A 1.25 Yes Power supply for various digital circuits							Power supply for SXR and AFE LDOS's.		
	1								

A — A= for analog circuits; D= for digital circuits

B— it is recommended to use 1.4 V for RF frequencies above 2.8 GHz

C—voltage level depends on the reference clock interface requirements.

^D – voltage level depends on the I/O post-driver requirements. Datasheet specifications guaranteed only at 3.3 V

1.3 Supply option description

LMS7002M chip has two power supply options:

- 1. Multiple supply option chip is powered by using several external power supply sources that generate 1.25V, 1.4V and 1.8V (optional 3.3V for digital input/output drivers);
- 2. Single supply option chip is powered by using a single external 1.8V power source (optional 3.3V for digital input/output drivers).

As the name implies, multiple supply option uses several external supply power sources to generate the required voltage levels for the LMS7002M. The main disadvantage of this mode is the requirement for additional on-board components. Nonetheless, multiple supply option also provides several key advantages:

- 1. Higher efficiency regulators (for example, switched mode) can be used to reduce the overall power consumption of the system;
- 2. Maximum digital interface speeds that are given in the datasheet can only be reached by using external power supplies for the digital blocks of LMS7002M;

Single supply option uses a single 1.8V external power source – additional regulator can be used if digital pad driver I/O levels need to be of a different voltage. In this mode, all low voltage power supply pins generate their 1.25V and 1.4V supplies from the 1.8V power source using internal LDOs. A more detailed analysis of this option is presented in *Section 2.2*. Note, that the single power supply option is not suited for applications that might use the LMS7002M chip in Multiple-In-Multiple-Out (MIMO) configuration with full digital processing capabilities (see *Section 2.2*). Nonetheless, single supply option also provides several key advantages:

- 1. Dynamic low voltage power supply pin scaling for fine tuning and optimization;
- 2. Reduced Bill of Materials (BOM) cost and board size.

2

Supply pin connection

2.1 Connection to multiple external supply sources

Table 2 shows the power supply pin connection requirements and current consumption when all LMS7002M chip power supplies are generated on board from multiple power sources. Since some pins can be connected in several ways depending on multiple requirements, their connection options are given in a separate tab with default (recommended) values. Typical power pin grouping and LDO recommendations are shown in Figure 2.

Board related power supply connection guidelines and notes are presented in Section 3.

Table 2: LMS7002M pin connection to multiple external supply sources

Pin ID	Pin Name	Supply rail, V		current ption, mA	Connection options
ID		ran, v	Typical ^A	Maximum ^B	•
J5	VDD12O_VCO_SXT	1.25		< 1	Connect to pin K6 (default) Do not connect, leave floating
K6	VDD12_VCO_SXT	1.25	20	40	
L5	VDD_DIV_SXT	1.4	10	20	Connect to 1.4V rail for maximum RF performance (default) Connect to 1.25V rail if RF frequency will not exceed 2.8GHz
K2	VDDO_DIV_SXT	1.4		< 1	Connect to pin L5 (default) Do not connect, leave floating
J3	VDD_CP_SXT	1.25	3	10	
M4	DVDD_SXT	1.25	5	10	
G3	VDD18_VCO_SXT	1.8	30	80	
B16	VDD_TPAD_TRF	1.25	5	10	
F8	VDD_TLOBUF_TRF	1.25	90	120	
D6	VDDO_TLOBUF_TRF	1.25		< 1	Connect to pin F8 (default) Do not connect, leave floating
D16	VDD18_TRF	1.8	20	80	
P4	VDD_TBB	1.25	30	80	
G5	VDD12_TXBUF	1.25	5	10	
Н6	VDD18_TXBUF	1.8	2	10	Connect to 1.8V (default) Connect to any other supply rail in the range of 1.8-3.3V according to the reference clock interface requirements
AN23	VDD12_VCO_SXR	1.25	20	40	
AM20	VDD_DIV_SXR	1.25	10	20	
AL19	VDD_CP_SXR	1.25	3	10	
AL21	DVDD_SXR	1.25	5	10	
AK22	VDD18_VCO_SXR	1.8	30	80	
AF6	VDD14_LNA_RFE	1.4	40	60	

Pin		Supply		current	
ID	Pin Name	rail, V		ption, mA	Connection options
		, , , , , , , , , , , , , , , , , , ,	Typical ^A	Maximum ^B	
AG5	VDD12_LNA_RFE	1.25	5	10	
AF2	VDD14_TIA_RFE	1.4	20	60	
AD6	VDD12_TIA_RFE	1.25	5	10	
AN17	VDD_MXLOBUF_RFE	1.4	140	180	Connect to 1.4V rail for maximum RF performance (default) Connect to 1.25V rail if RF frequency will not exceed 2.8GHz
AD4	VDD14_RBB	1.4	40	80	
AP26	VDD12_RXBUF	1.25	5	10	
AM26	VDD18_RXBUF	1.8	2	10	Connect to 1.8V (default) Connect to any other supply rail in the range of 1.8-3.3V according to the reference clock interface requirements
C21	VDD14_VCO_CGEN	1.4	5	10	
F20	VDD_CP_CGEN	1.25	3	5	
E19	VDD_DIV_CGEN	1.25	5	10	
A17	DVDD_CGEN	1.25	5	10	
E21	VDD18_VCO_CGEN	1.8	5	10	
AJ25	VDD_AFE	1.25	80	120	
E17	VDD18_BIAS	1.8	12	20	
F24	VDD_SPI_BUF	1.25	5	5	
AE29	DIGPRVDD1	1.25	100	400	
AA29	DIGPRVDD1	1.25			
R31	DIGPRVDD1	1.25	50	250	
L33	DIGPRVDD1	1.25			
AH30	DIGPRVDD2	3.3	20	120	
W33	DIGPRVDD2	3.3			1 0 44 22876
W31	DIGPRPOC	3.3			1. Connect to 3.3V for maximum digital interface performance
H32	DIGPRVDD2	3.3	20	120	2. Connect to any other supply rail in the range of 1.8-3.3V according to the digital interface requirements
T32	DIGPRVDD2, DIGPRPOC	3.3			according to the digital interface requirements
N1	VDD18 LDO TX	1.8	2	5	
AE3	VDD18 TIA RFE	1.8	2	5	
AF4	VDD18 LDO RX	1.8	2	5	
AM18	VDD18 SXR	1.8	2	5	
C25	VDD12 DIG	1.25	2	5	
D24	VDD18_DIG	1.8	2	5	

A – LMS7002M is configured in FDD MIMO mode, with 30.72MHz IF bandwidth and a carrier frequency that does not exceed 2.6GHz

B – conditional maximum pin current consumption

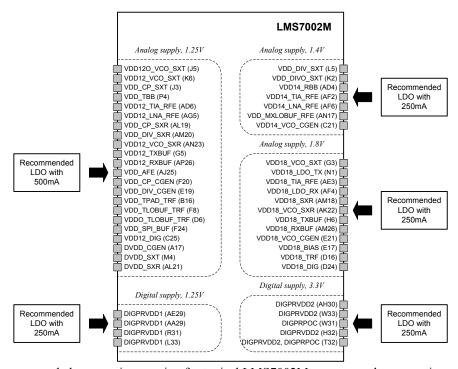


Figure 2. Recommended power pin grouping for typical LMS7002M power supply connection with multiple power sources

2.2 Connection to single external supply

When LMS7002M is used from a single power supply rail, several key features must be implemented in the designed board and in the software control:

- 1. Low voltage power pins (1.25V and 1.4V) should be connected to a 1μF capacitor that is connected to ground for stable internal LDO operation. Note, that for grouped pins, that require external connection to one another (see Figure 1), only one capacitor is needed per group;
- 2. CORE_LDO_EN (U33) pin needs to be tied to VDD (minimum 1.8V) or left unconnected (it has internal pull-up);
- 3. All internal LDO's need to be enabled. The required modifications for the Serial Peripheral Interface (SPI) memory map are listed in Table 3.

Address	Bits	Setting
0x0092	[15:0]	1111 1111 1111 1111
0x0093	[15:0]	0000 0011 1111 1111
0x0099	[15:0]	0110 0101 1000 1100
0x009E	[15:0]	1000 1100 1000 1100

Table 4 shows the power supply pin connection requirements and current consumption when all LMS7002M chip power supplies are generated on board from a single 1.8V power source. Note, that digital interface power pins may need to be connected to a different power source according to the digital interface requirements. Typical power pin grouping and LDO recommendations are shown in Figure 3.

As noted in Section 1.3, single external supply is not recommended when the digital TSP blocks of LMS7002M are used at their full processing capabilities. Full digital block processing capabilities are considered enabled when the chip is running in MIMO configuration with every TSP sub-block enabled, while TxTSP and RxTSP are running at 640MHz and 160MHz respectively. Typical max current consumptions for digital pins are given with TxTSP and RxTSP General Purpose Finite Impulse Response (GFIR) filters bypassed.

Board related power supply connection guidelines and notes are presented in Section 3.

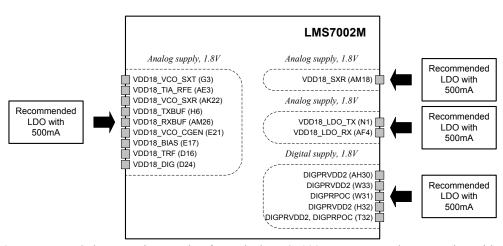


Figure 3. Recommended power pin grouping for typical LMS7002M power supply connection with a single power sources

Table 4: LMS7002M pin connection to a single external supply source

Pin ID	Pin Name	Supply rail, V		current otion, mA	Connection options
ш		ran, v	Typical ^A	Maximum ^B	
G3	VDD18_VCO_SXT		30	80	
D16	VDD18_TRF		20	80	
Н6	VDD18_TXBUF		7	20	
AK22	VDD18_VCO_SXR		30	80	
AM26	VDD18_RXBUF		8	21	
E21	VDD18_VCO_CGEN		27	49	
E17	VDD18_BIAS		12	20	
AH30	DIGPRVDD2				
W33	DIGPRVDD2	1.8	120	525	Connect to 1.8V for single power supply option
W31	DIGPRPOC	1.0			2. Connect to 3.3V for maximum digital interface performance
H32	DIGPRVDD2				3. Connect to any other supply rail in the range of 1.8-3.3V
T32	DIGPRVDD2,		70	375	according to the digital interface requirements
132	DIGPRPOC				
N1	VDD18_LDO_TX		170	300	
AE3	VDD18_TIA_RFE		2	5	
AF4	VDD18_LDO_RX		115	225	
AM18	VDD18_SXR		265	390	
D24	VDD18_DIG		10	20	

A – LMS7002M is configured in FDD MIMO mode, with 30.72MHz IF bandwidth and a carrier frequency that does not exceed 2.6GHz

B – conditional maximum pin current consumption

3

Recommendations for board design

3.1 Power supply pin connection

There are three recommended power supply pin connection types to the external voltage regulators. The connections are shown in Figure 4. The pin list, with recommended connection option is given in Table 5.

If the chip is run from internal LDOs, only the capacitor(s) directly connected to the low voltage LMS7002M pins should be used. They are needed to guarantee stable internal LDO operation.

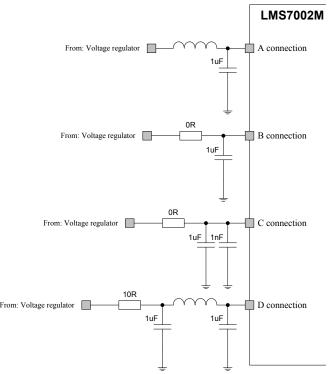


Figure 4. LMS7002M power pin connection to on-board LDOs options

Table 5: LMS7002M pin connection to multiple external supply sources

Pin ID	Pin Name	Connection option from Figure 4
J5	VDD12O_VCO_SXT	A
K6	VDD12_VCO_SXT	A
L5	VDD_DIV_SXT	
K2	VDDO_DIV_SXT	A
J3	VDD_CP_SXT	В
M4	DVDD_SXT	A
G3	VDD18_VCO_SXT	A
B16	VDD_TPAD_TRF	A
F8	VDD_TLOBUF_TRF	A
D6	VDDO_TLOBUF_TRF	A
D16	VDD18_TRF	A
P4	VDD_TBB	A
G5	VDD12_TXBUF	D
Н6	VDD18_TXBUF	D
AN23	VDD12_VCO_SXR	A
AM20	VDD_DIV_SXR	A
AL19	VDD_CP_SXR	В
AL21	DVDD SXR	A
AK22	VDD18_VCO_SXR	A
AF6	VDD14 LNA RFE	A
AG5	VDD12 LNA RFE	A
AF2	VDD14 TIA RFE	A
AD6	VDD12 TIA RFE	A
AN17	VDD MXLOBUF RFE	A
AD4	VDD14 RBB	A
AP26	VDD12 RXBUF	D
AM26	VDD18 RXBUF	D
C21	VDD14 VCO CGEN	A
F20	VDD CP CGEN	В
E19	VDD DIV CGEN	A
A17	DVDD_CGEN	A
E21	VDD18 VCO CGEN	A
AJ25	VDD AFE	A
E17	VDD18 BIAS	A
F24	VDD_SPI_BUF	A
AE29	DIGPRVDD1	С
AA29	DIGPRVDD1	С
R31	DIGPRVDD1	C
L33	DIGPRVDD1	C
AH30	DIGPRVDD2	C
W33	DIGPRVDD2	C
W31	DIGPRPOC	C
H32	DIGPRVDD2	C
T32	DIGPRVDD2, DIGPRPOC	C
N1	VDD18 LDO TX	A
AE3	VDD18 TIA RFE	A
AF4	VDD18_LDO_RX	A
AM18	VDD18_EDG_RX VDD18_SXR	A
C25	VDD10_SAR	A
023	VDD12_DIG VDD18_DIG	A

When selecting and LDO's, keep attention to the power-supply rejection ratio (PSRR) and the output noise. The PSSR should be $>\!60dB$ at 1kHz, while the output noise should be $>\!0.25\mu V\sqrt{Hz}$ at 1KHz.

3.2 TX power amplifier supply connection

TX power amplifier (PA) is supplied from its output pins from a 1.8V source. A typical TX output connection is shown in Figure 5. The inductor and matching network values depend on desired output frequency. There are two power amplifier outputs per TX channel and only one can be working at a time. The maximum power supply requirement per channel is 100mA (MIMO mode 200mA), with a typical value close to 70mA (MIMO mode 140mA).

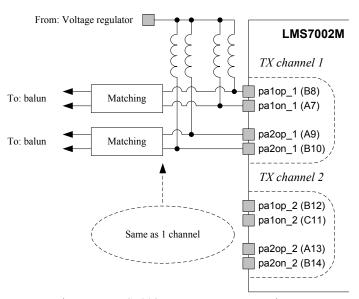


Figure 5. LMS7002M TX output connection